 


第十章综合设计实例

1 键盘扫描与显示


- 矩阵式键盘:行,列



矩阵是键盘以行列形式排列，键盘上每个按键其实是一个开关电路，当某键被按下时，该按键对应的位置就呈现逻辑0状态。

行扫描方式:逐行送0电平,读取列的状态,以判断按下的键号.

列扫描方式:逐列送0电平,读取行的状态,以判断按下的键号.

 


以行扫描为例

1给行依次送0111,1011,1101,1110 信号;

2读取列电平状态

数码管显示

 

按键扫描控制程序

- library ieee;
- use ieee.std_logic_1164.all;
- use ieee.std_logic_unsigned.all;
- entity key_scan is
- port(column:in std_logic_vector(3 downto 0); -- 列状态
- scan_cnt:in std_logic_vector(3 downto 0);--- 扫描字
- row:out std_logic_vector(3 downto 0);--- 行状态
- key_pressed:out std_logic);----- 按键有效与否后续判断为零则为有键按下
- end ;
- architecture rtl of key_scan is
- begin
- row<="1110" when scan_cnt(3 downto 2)="00" else
- "1101" when scan_cnt(3 downto 2)="01" else
- "1011" when scan_cnt(3 downto 2)="10" else
- "0111";
- key_pressed<=column(0) when scan_cnt(1 downto 0)="00" else
- column(1) when scan_cnt(1 downto 0)="01" else
- column(2) when scan_cnt(1 downto 0)="10" else
- column(3);
- end rtl ;

按键处理控制模块

- library ieee;
- use ieee.std_logic_1164.all;
- use ieee.std_logic_unsigned.all;
- use ieee.std_logic_arith.all;
- entity scan_count is
- port(clk:in std_logic;--clock
- scan_clk:in std_logic;--1khz clk
- key_pressed:in std_logic;--检测按键有效与否,停止计数.
- scan_cnt:out std_logic_vector(3 downto 0));--计数
- end;

- architecture behav of scan_count is
- signal qscan:std_logic_vector(3 downto 0);
- begin
- scan_1:process(clk,scan_clk,key_pressed)
- begin
- if(clk'event and clk='1')then
- if(scan_clk='1' and key_pressed='1')then
- qscan<=qscan+1; end if; end if;
- end process;
- scan_cnt<=qscan; end;

按键消抖控制模块

- **library ieee;**
- **use ieee.std_logic_1164.all;**
- **use ieee.std_logic_unsigned.all;**
- **use ieee.std_logic_arith.all;**
- **entity debounce is**
- **port(key_pressed:in std_logic;**
- **clk:in std_logic;-- 同步时钟**
- **scan_clk:in std_logic;--1khz clock**
- **key_valid:out std_logic);**
- **end;**
- **architecture behav of debounce is**
- **begin**
-

- **debounce:process(clk,scan_clk,key_pressed)**
- **variable dbnq:std_logic_vector(5 downto 0);**
- **begin**
- **if(key_pressed='1')then**
- **dbnq:="111111";--unkey_pressed,count reset at 63**
- **elsif(clk'event and clk='1')then**
- **if scan_clk='1' then**
- **if dbnq/=1 then**
- **dbnq:=dbnq-1;--key_pressed not enough long time**
- **end if; end if; end if;**
- **if dbnq=2 then**
- **key_valid<='1';--key_valid after key_pressed 1/63k second**
- **else**
- **key_valid<='0';**
- **end if;**
- **end process;**
- **end;**

键盘译码及按键存储模块

- **library ieee;**
- **use ieee.std_logic_1164.all;**
- **use ieee.std_logic_unsigned.all;**
- **use ieee.std_logic_arith.all;**
- **entity code_tran is**
- **port(clk:in std_logic;--clock for synchrony**
- **scan_cnt:in std_logic_vector(3 downto 0);--1khz clock**
- **key_valid:in std_logic;**
- **butt_code:out std_logic_vector(3 downto 0));**
- **end;**

- **architecture bb of code_tran is**
- **begin**
- **process(clk)**
- **begin**
- **if(clk'event and clk='1')then**
- **if key_valid='1' then**
- **case scan_cnt is**

- **when "0000" => butt_code <= "0001";--1**
- **when "0001" => butt_code <= "0010";--2**
- **when "0010" => butt_code <= "0011";--3**
- **when "0011" => butt_code <= "1100";--c**
- **when "0100" => butt_code <= "0100";--4**
- **when "0101" => butt_code <= "0101";--5**
- **when "0110" => butt_code <= "0110";--6**
- **when "0111" => butt_code <= "1101";--d**
- **when "1000" => butt_code <= "0111";--7**
- **when "1001" => butt_code <= "1000";--8**
- **when "1010" => butt_code <= "1001";--9**
- **when "1011" => butt_code <= "1110";--e**
- **when "1100" => butt_code <= "1010";--a**
- **when "1101" => butt_code <= "0000";--0**
- **when "1110" => butt_code <= "1011";--b**
- **when others => butt_code <= "1111";--f**
- **end case;**
- **end if; end if;**
- **end process;end ;**

电锁控制模块

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity ctrl is
    port(data_n:in std_logic_vector(3 downto 0);
          key_valid,clk:in std_logic;
          enlock:out std_logic;
          d,c,b,a:out std_logic_vector(3 downto 0));
end;
```

```
architecture aaa of ctrl is
    signal acc,reg:std_logic_vector(15 downto 0);
    signal nc:std_logic_vector(2 downto 0);
    signal qa,qb:std_logic;
begin
    keyin:block is
        begin
            process(data_n,key_valid)
```

```

begin
    if data_n="1101" then
        acc<="0000000000000000";
        nc<="000";
    elsif key_valid'event and key_valid='1' then
        if data_n<"1101" then
            if nc<=4 then
                acc<=acc(11 downto 0)&data_n;
                nc<=nc+1;
            end if;end if;end if;end process;end block;
lock:block is
    begin
        process(clk,data_n)
        begin
            if(clk'event and clk='1')then
                if nc=4 then
                    if data_n="1110" then
                        reg<=acc;
                        qa<='1';qb<='0';
                    elsif data_n="1111" then
                        if reg=acc then
                            qa<='0';qb<='1';
                        end if;end if;end if;end if;end process;end block;

```

- enlock<=qa and not qb;
- d<=acc(15 downto 12);
- c<=acc(11 downto 8);
- b<=acc(7 downto 4);
- a<=acc(3 downto 0);
- end aaa;


动态扫描显示控制模块

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity sel_display is
port(clk:in std_logic;
      d,c,b,a:in std_logic_vector(3 downto 0);
      db_out:out std_logic_vector(3 downto 0);
      dis_out:out std_logic_vector(3 downto 0));
end entity;

architecture rtl of sel_display is
  signal sel:std_logic_vector(1 downto 0);
  signal dis:std_logic_vector(3 downto 0);
  signal db:std_logic_vector(3 downto 0);
begin
```

```
counter:block is
  signal q:std_logic_vector(6 downto 0);
  begin
    process(clk)
    begin
      if clk'event and clk='1' then
        q<=q+1;
      end if;
    end process;
    sel<=q(1 downto 0);
  end block counter;
```
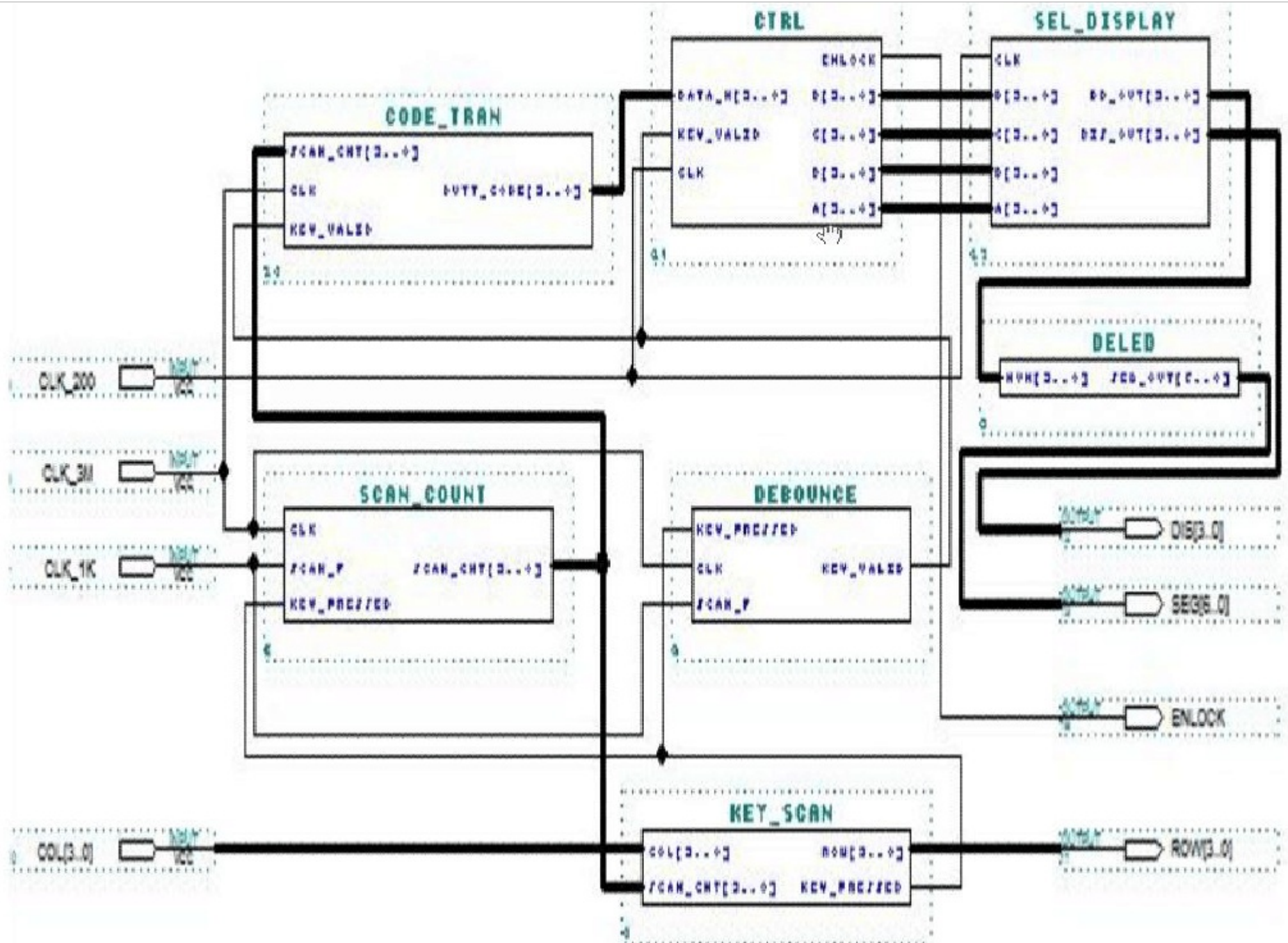
```
multiplexer:block is
begin
  process(sel)
  begin
    if sel=0 then
      db<=d;  dis<="0111";
    elsif sel=1 then
      db<=c;  dis<="1011";
    elsif sel=2 then
      db<=b;  dis<="1101";
    elsif sel=3 then
      db<=a;  dis<="1110";
    end if;
  end process;
end block multiplexer;
db_out<=db;
dis_out<=dis;
end rtl;
```





实例1 数字钟设计

实时显示时、分、秒

分析：

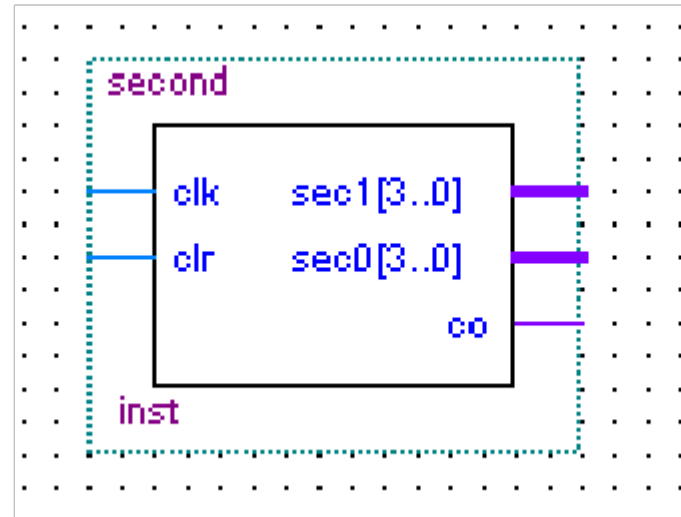- 1、最小计时单位：秒。因此，首先要由时钟产生1Hz的信号；
- 2、对秒进行0-59的计数，并且有进位功能，且显示；
- 3、对分进行0-59的计数，并且有进位功能，且显示；
- 4、对时进行0-59的计数，且显示；



```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all
entity second is
    port(clk,clr:in std_logic;--clk=1Hz
          sec1,sec0:out std_logic_vector(3 downto 0);
          co:out std_logic );
end second;
architecture arch of second is
begin

process(clk,clr)
    variable cnt1,cnt0:std_logic_vector(3 downto 0);
begin
    if clr='0' then
        cnt1:="0000";
        cnt0:="0000";
    elsif clk'event and clk='1' then
        if cnt1="0101" and cnt0="1000" then co<='1';
            cnt0:="1001";
        elsif cnt0<"1001" then
            cnt0:=cnt0+1;

```

```

else
        cnt0:="0000";
    if cnt1<"0101" then
        cnt1:=cnt1+1;
    else
        cnt1:="0000";
        co<='0';
        end if;
    end if;
end if;


        sec1<=cnt1;
        sec0<=cnt0;
    end process;
end arch;

```

实例2 出租车计费器设计


功能:

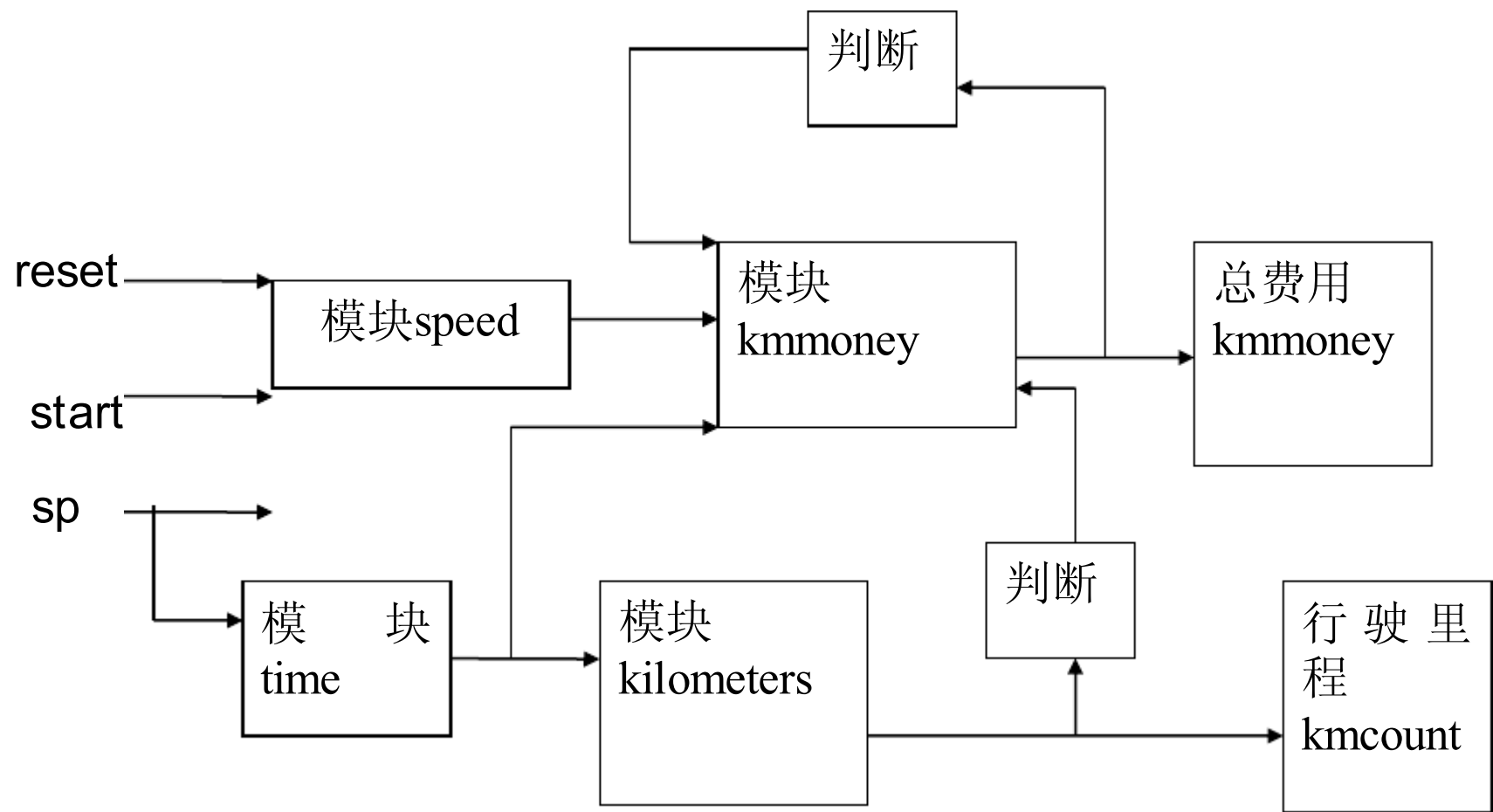- (1) 实现计费功能。车起步开始计费, 首先显示起步价, 设起步费为8.00元, 车在行驶3 km以内, 只收起步费8.00元。车行驶超过3 km后, 每公里2元, 车费依次累加。当总费用达到或超过10元时, 每公里收费4元。当遇到红灯或客户需要停车等待时, 则按时间计费, 计费单价为每20S收费1元。
- (2) 实现预置功能: 预置起步费、每公里收费、车行加费里程、计时收费。
- (3) 实现模拟功能: 模拟汽车行驶、停止、暂停等状态。
- (4) 实现显示功能: 将路程与车费显示出来, 以十进制显示。




系统流程如下：

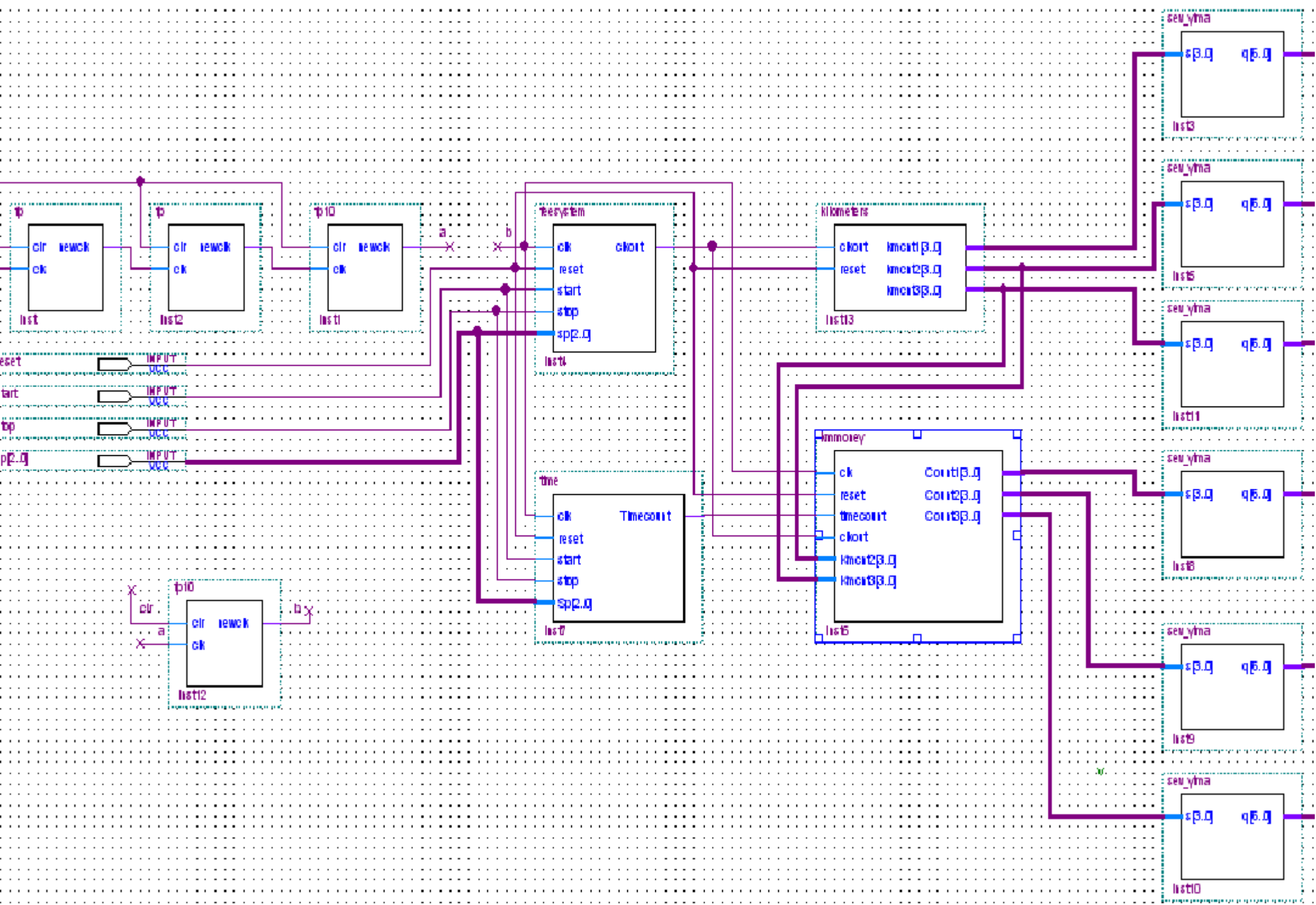- (1) 系统接收到**reset**信号后，总费用变为8元，同时其他计数器，寄存器等全部清零。
- (2) 系统接收到**start**信号后，首先把部分寄存器赋值，总费用不变，单价**price**寄存器通过对总费用的判断后赋为2元。其他寄存器和计数器等继续保持为0。
- (3) **speed**进程：通过对速度信号**sp**的判断，决定变量**kinside**的值。**kinside**即是行进100m所需要的时钟周期数，然后每行进100m，则产生一个脉冲**clkout**。
- (4) **kilometers**进程：由于一个**clkout**信号代表行进100m，故通过对**clkout**计数，可以获得共行进的距离**kmcount**。
- (5) **time**进程：在汽车启动后，当遇到顾客等人或红灯时，出租车采用计时收费的方式。通过对速度信号**sp**的判断决定是否开始记录时间。当**sp=0**时，开始记录时间。当时间达到足够长时则产生**timecount**脉冲，并重新计时。一个**timecount**脉冲相当于等待的时间达到了时间计费的长度。这里选择系统时钟频率为500Hz，20s即计数值为1000。
- (6) **kmmoney**可分为**kmmoney1**和**kmmoney2**两个进程。
 - kmmoney1**进程：根据条件对**enable**和**price**赋值。当记录的距离达到3公里后**enable**变为‘1’，开始进行每公里收费，当总费用大于40元后，则单价**price**由原来的2元每公里变为4元每公里。
 - kmmoney2**进程：在每个时钟周期判断**timecount**和**clkout**的值。当其为‘1’时，则在总费用上加上相应的费用。



speed 模块

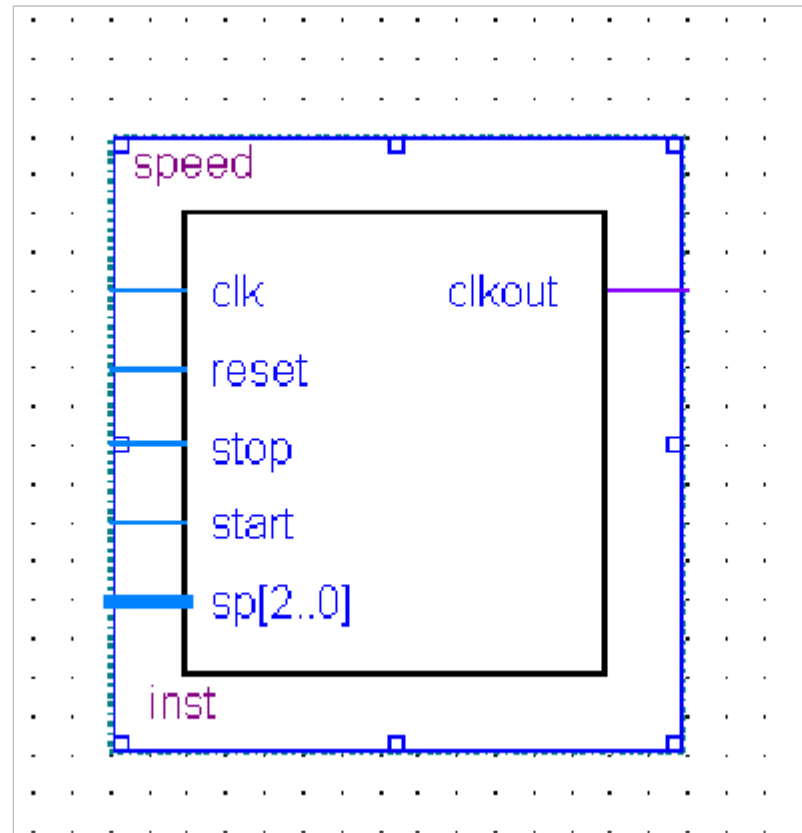speed 进程首先根据**start**信号判断是否开始计费，然后根据输入的速度档位**sp[2..0]** 的判断，确定行驶**100M**所需要的时钟数，每前进**100M**，输出一个**clkout** 信号。同时由**cnt**对**clk**进行计数，当**cnt=kinside** 时，把**clkout** 信号置 '1'，**cnt** 清0。



```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity feesystem is
  Port(clk:in std_logic;
        reset:in std_logic;
        start: in std_logic;
        stop: in std_logic;
        sp:in std_logic_vector(2 downto 0);
        clkout:out std_logic);
end feesystem;
architecture behav of feesystem is
begin
  process(clk,reset,stop,start,sp)
    type state_type is(s0,s1);
    variable s_state:state_type;
    variable cnt:integer range 0 to 28;
    variable kinside:integer range 0 to 30;
  begin
    case sp is
      ---7档速度选择，具体每档kinside的值可根据实际情况设定
      when "000"=> kinside:=0;  -- 停止状态或空挡

```

when "001"=> kinside:=28; -- 第一档，慢速行驶状态，行驶100m需要28个时钟周期

when "010"=> kinside:=24; -- 第二档

when "011"=> kinside:=20; -- 第三档

when "100"=> kinside:=16; -- 第四档

when "101"=> kinside:=12; -- 第五档

when "110"=> kinside:=8; -- 第六档

when "111"=> kinside:=4; -- 第七档，也是速度最大的档

end case;

if reset='1'then s_state:=s0;

elsif clk'event and clk='1'then

case s_state is

when s0=>

cnt:=0;clkout<='0';

if start='1'then s_state:=s1;

else s_state:=s0;

end if;

when s1=>

clkout<='0';

if stop='1' then s_state:=s0; --相当于无客户上车

elsif sp="000" then s_state:=s1; ---有客户上车，但车速位0，即客户刚上车还未起步

elsif cnt=kinside then cnt:=0;clkout<='1'; s_state:=s1;

else cnt:=cnt+1; s_state:=s1;


end if;

end case;

end if;


end process;

end behav;

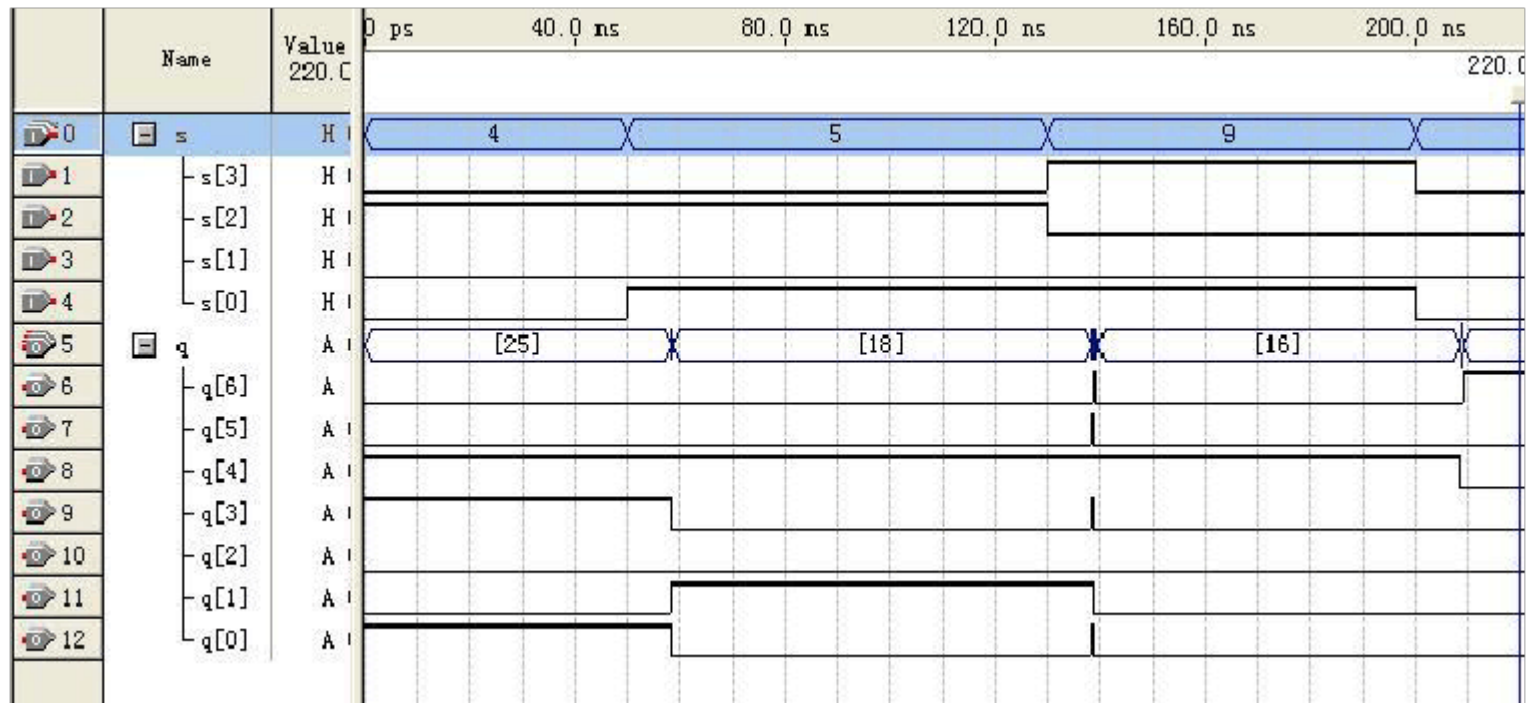

kilometers 模块

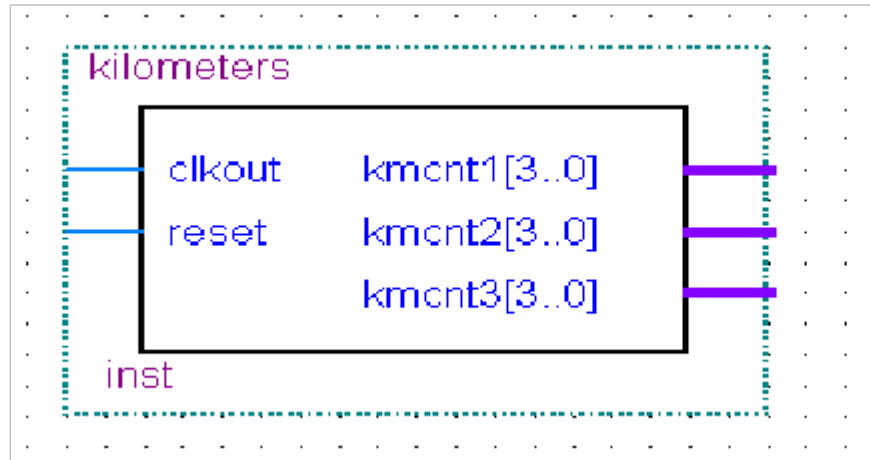此模块主要用于记录行进的距离。通过~~clkout~~ **clkout** 信号的计数，可以计算行驶的距离~~kmcount~~ **kmcount**。一个**clkout** 脉冲相当于行进**100m**，所以只要记录**clkout** 的脉冲数目即可确定共行进的距离。**kmcount1** 为十分位，**kmcount2** 为个位，**kmcount3** 为十位，分别为十进制数。



```

Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity kilometers is
    Port(clkout,reset:in std_logic;
          kmcnt1:out std_logic_vector(3 downto 0);
          kmcnt2:out std_logic_vector(3 downto 0);
          kmcnt3:out std_logic_vector(3 downto 0));
end kilometers;
architecture behav of kilometers is
begin
    process(clkout,reset)
        variable km_reg:std_logic_vector(11 downto 0);
    begin
        if reset='1'then km_reg:="000000000000";
        elsif clkout'event and clkout='1'then          --km_reg(3 downto 0)对应里程十分
    位

```



```
if km_reg(3 downto 0)="1001"then
```

```
    km_reg:=km_reg+"0111";
```

--十分位向个位的进位处理

```
else km_reg(3 downto 0):=km_reg(3 downto 0)+"0001";
```

```
end if;
```

```
if km_reg(7 downto 4)="1010"then
```

```
    km_reg:=km_reg+"01100000";
```

--个位向十位的进位处理

```
end if;
```

```
end if;
```


```
kmcnt1<=km_reg(3 downto 0);
```

```
kmcnt2<=km_reg(7 downto 4);
```

```
kmcnt3<=km_reg(11 downto 8);
```

```
end process;
```


```
end behav;
```

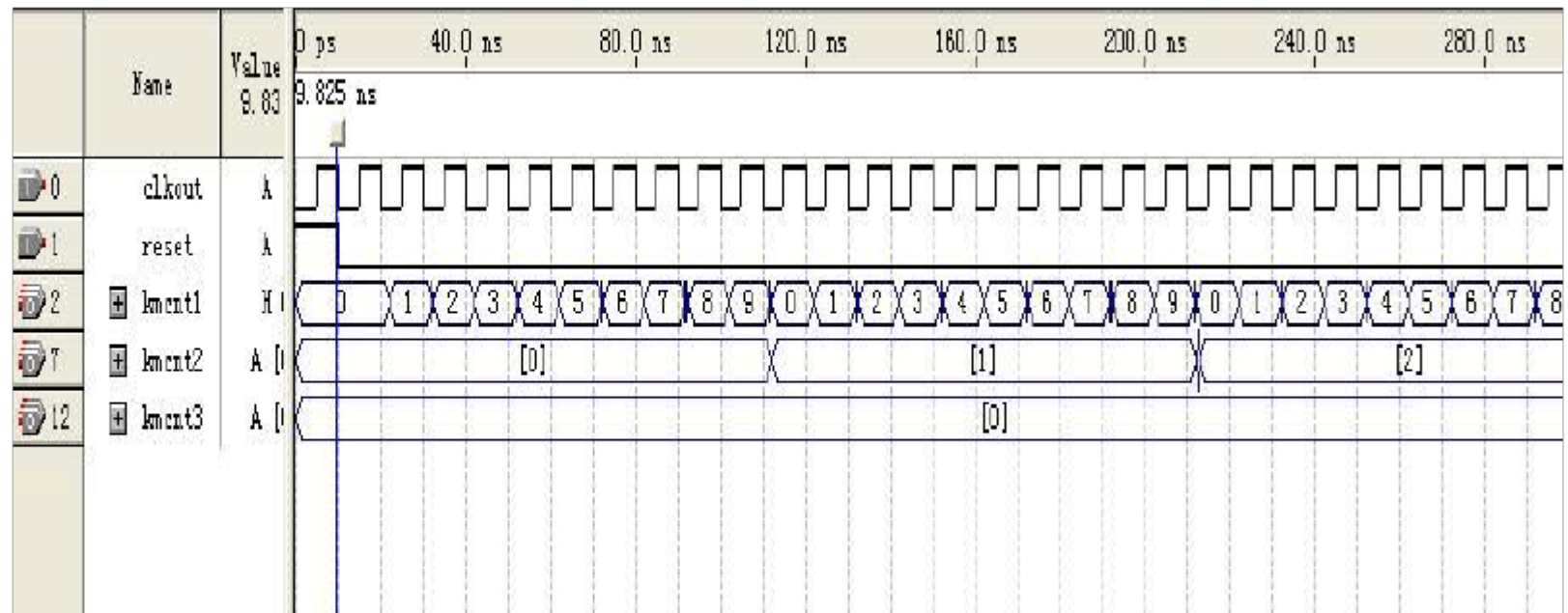

time模块

time模块主要用于计时收费。记录计程车速度为0的时间（如等待红灯）。通过对sp信号的判断，当sp=0，开始记录时间。当时间达到足够长时，产生timecount脉冲，并重新计时。

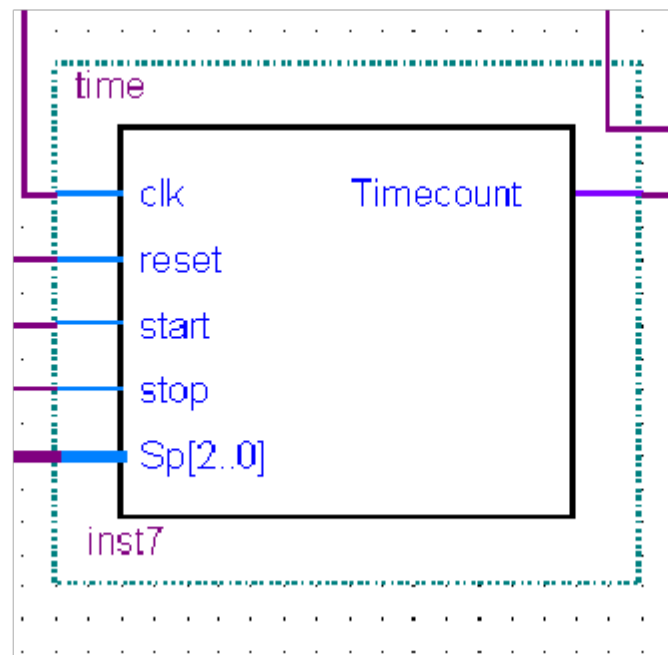time进程，产生时间计费脉冲timecount，单位计费时间可设定，这里选为20s



```
Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity time is
    Port(clk,reset,start,stop:in std_logic;
          Sp:in std_logic_vector(2 downto 0);
          Timecount:out std_logic);
End time;
architecture behav of time is
begin
    process(reset,clk,sp,stop,start)
        type state_type is(t0,t1,t2);
        variable t_state:state_type;
        variable waittime: integer range 0 to 1000;
    begin
        if reset='1'then t_state:=t0;
        elsif(clk'event and clk='1')then
```

```


case t_state is
  when t0 =>
    waittime:=0;timecount<='0';
    if start='1'then t_state:=t1;
    else t_state:=t0;
    end if;
  when t1 =>
    if sp="000"then t_state:=t2;
    else waittime:=0;t_state:=t1;
    end if;
  when t2 =>
    waittime:=waittime+1;
    timecount<='0';
    if waittime=1000 then
      timecount<='1';    --20s,即1000个clk, 产生一个时间计费脉冲
      waittime:=0;
    elsif stop='1'then t_state:=t0;
    elsif sp="000"then t_state:=t2;
    else timecount<='0';t_state:=t1;
    end if;
  end case;
end if;
end process;
end behav;

```

kmmoney 模块

kmmoney 可分为kmmoney1 和kmmoney2 两个模块。

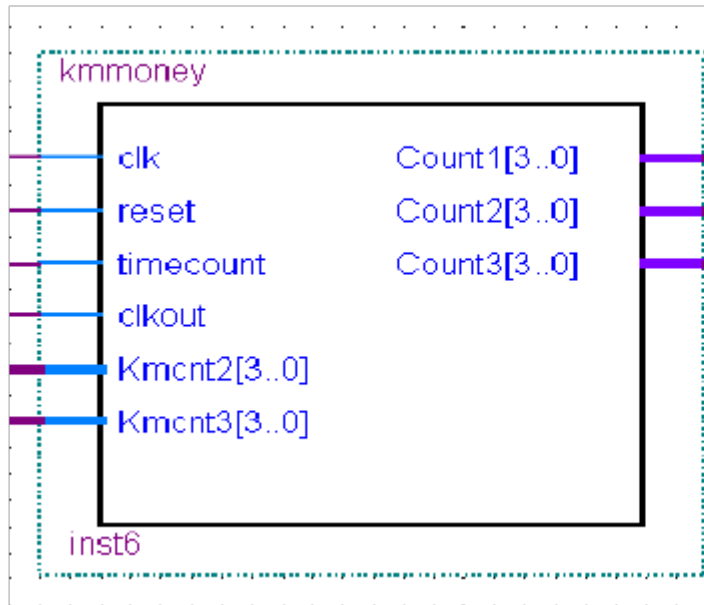kmmoney1 用于产生enable 和price 信号。当记录距离达到3公里后，enable 信号为 '1'，开始进行每公里的收费。当总费用为40元后，单价price 由原来的2元变为4元。用作计时收费。通过sp 信号的判断，当sp=0，开始记录时间。当时间达到足够长时，产生timecount 脉冲，并重新计时。kmmoney2 用于判断timecount 和clkout 的值，当其为 '1'时，总费用加。最终输出为总费用。



计费采用两个进程kmmoney1 和kmmoney2 实现;
总费用上限位999元，一旦超过上限，显示会出现不正常现象

```
Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_unsigned.all;
Entity kmmoney is
    Port(clk,reset,timecount,clkout:in std_logic;
          Kmcnt2:in std_logic_vector(3 downto 0);
          Kmcnt3:in std_logic_vector(3 downto 0);
          Count1:out std_logic_vector(3 downto 0);
          Count2:out std_logic_vector(3 downto 0);
          Count3:out std_logic_vector(3 downto 0));
End kmmoney;
Architecture behav of kmmoney is
Signal cash:std_logic_vector(11 downto 0);
Signal price:std_logic_vector(3 downto 0);
Signal enable: std_logic;
Begin
    Process(cash,kmcnt2)
    Begin
        If cash>="000001000000"then price<="0100";
        Else price<="0010";
        End if;
```

```


If(kmcnt2>="0011")or(kmcnt3>="0001")then enable<='1';
  Else enable<='0';
  End if;
End process;
kmmoney2:process(reset,clkout,clk,enable,price,kmcnt2)
variable reg2:std_logic_vector(11 downto 0);
variable clkout_cnt:integer range 0 to 10;
begin
  if reset='1' then cash<="000000001000";  -- 起步费用设为8元
  elsif clk'event and clk='1' then
    if timecount='1' then                    -判断是否需要时间计费，每20s加一元
      reg2:=cash;
      if reg2(3 downto 0)+"0001">"1001" then
        reg2(7 downto 0):=reg2(7 downto 0)+"00000111";
        if reg2(7 downto 4)>"1001" then
          cash <=reg2+"000001100000";
        else cash<=reg2;
        end if;
      else cash<=reg2+"0001";
      end if;
    elsif clkout='1' and enable='1' then      --里程计费

```

```

if clkout_cnt=9 then
    clkout_cnt:=0;
    reg2:=cash;
    if"0000"@2(3 downto 0)+price(3 downto 0)>"00001001"then
        reg2(7 downto 0):=reg2(7 downto 0)+"00000110"+price;
        if reg2(7 downto 4)>"1001"then
            cash<=reg2+"000001100000";
        else cash<=reg2;
        end if;
    else cash<=reg2+price;
    end if;
else clkout_cnt:=clkout_cnt+1;
end if;
end if;
end if;
end process;
count1<=cash(3 downto 0);    --总费用的个位
count2<=cash(7 downto 4);    --总费用的十位
count3<=cash(11 downto 8);   --总费用的百位
End behav;



```

 分频模块

对系统的时钟进行分频，以模拟轮胎的滚动。


(a) 100分频 (b)10分频

  

```
Library ieee;
Use ieee.std_logic_1164.all;
entity fp is
    port(clr,clk:in std_logic;
          newclk:out std_logic);
end fp;
architecture behav of fp is
    signal tem:integer range 0 to 99;
begin
    process(clk,clr)
    begin
        if(clr='1')then
            tem<=0;
            newclk<='0';
        elsif(clk'event and clk='1')then
            if(tem=99)then
                tem<=0;
                newclk<='1';
            else tem<=tem+1;
                newclk<='0';
            end if;
        end if;
    end process;
end behav;
```

```
Library ieee;
Use ieee.std_logic_1164.all;
entity fp10 is
    port(clr,clk:in std_logic;
          newclk:out std_logic);
end fp10;
architecture behav of fp10 is
    signal tem:integer range 0 to 9;
begin
    process(clk,clr)
    begin
        if(clr='1')then
            tem<=0;
            newclk<='0';
        elsif(clk'event and clk='1')then
            if(tem=9)then
                tem<=0;
                newclk<='1';
            else tem<=tem+1;
                newclk<='0';
            end if;
        end if;
    end process;
end behav;
```


显示模块

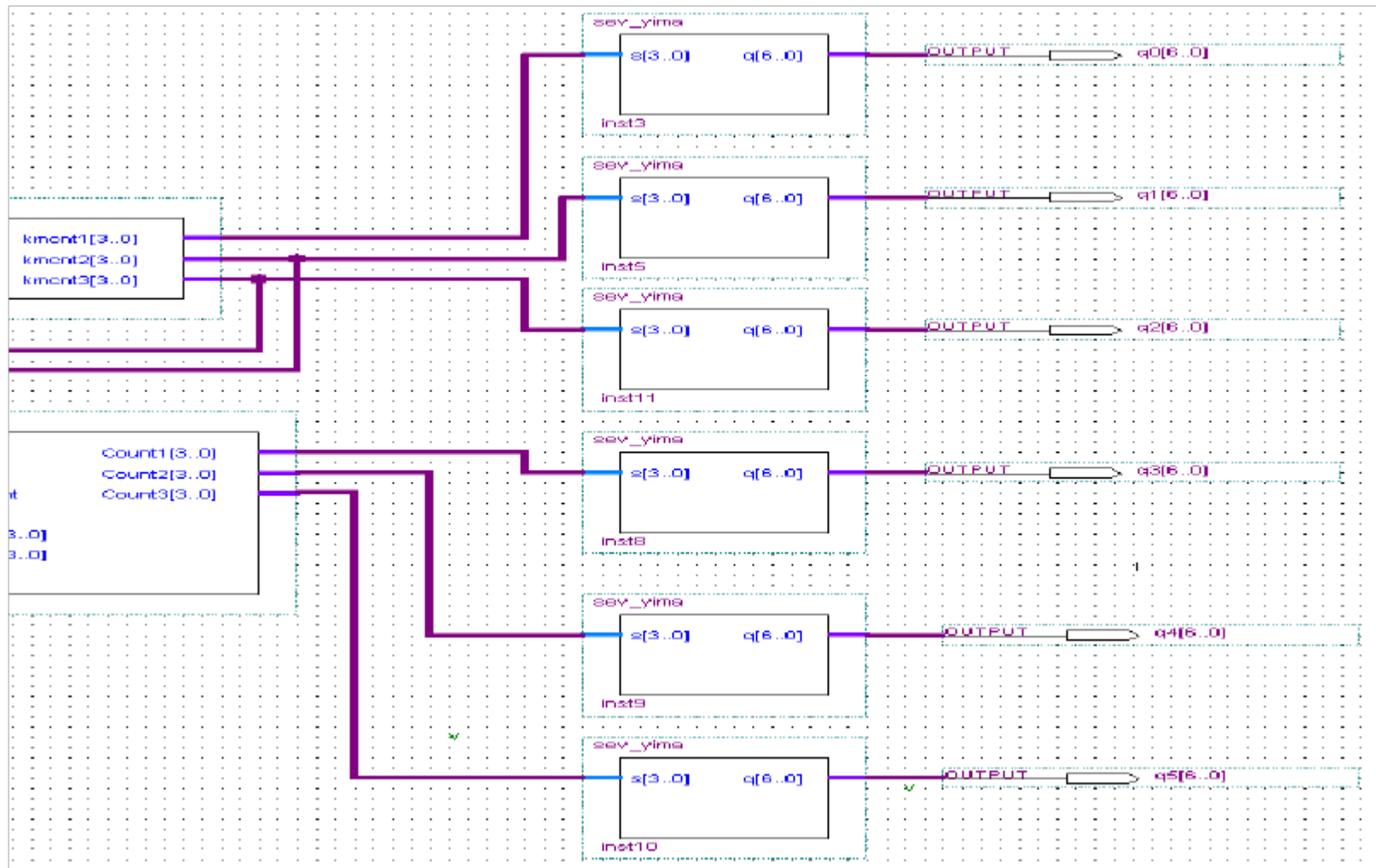

```
library ieee;
use ieee.std_logic_1164.all;
entity sev_yima is
port(s:in std_logic_vector(3 downto 0);
     q:out std_logic_vector(6 downto 0));
end sev_yima;
architecture rtl of sev_yima is
begin
    with s select
        q<= "1000000"when "0000",
            "1111001"when "0001",
            "0100100"when "0010",
            "0110000"when "0011",
            "0011001"when "0100",
            "0010010"when "0101",
            "0000010"when "0110",
            "1111000"when "0111",
            "0000000"when "1000",
            "0010000"when "1001",
            "1111111"when others;
end rtl;
```


实例3 频率计设计

- 要求：对输入信号进行频率的测量并实时显示。

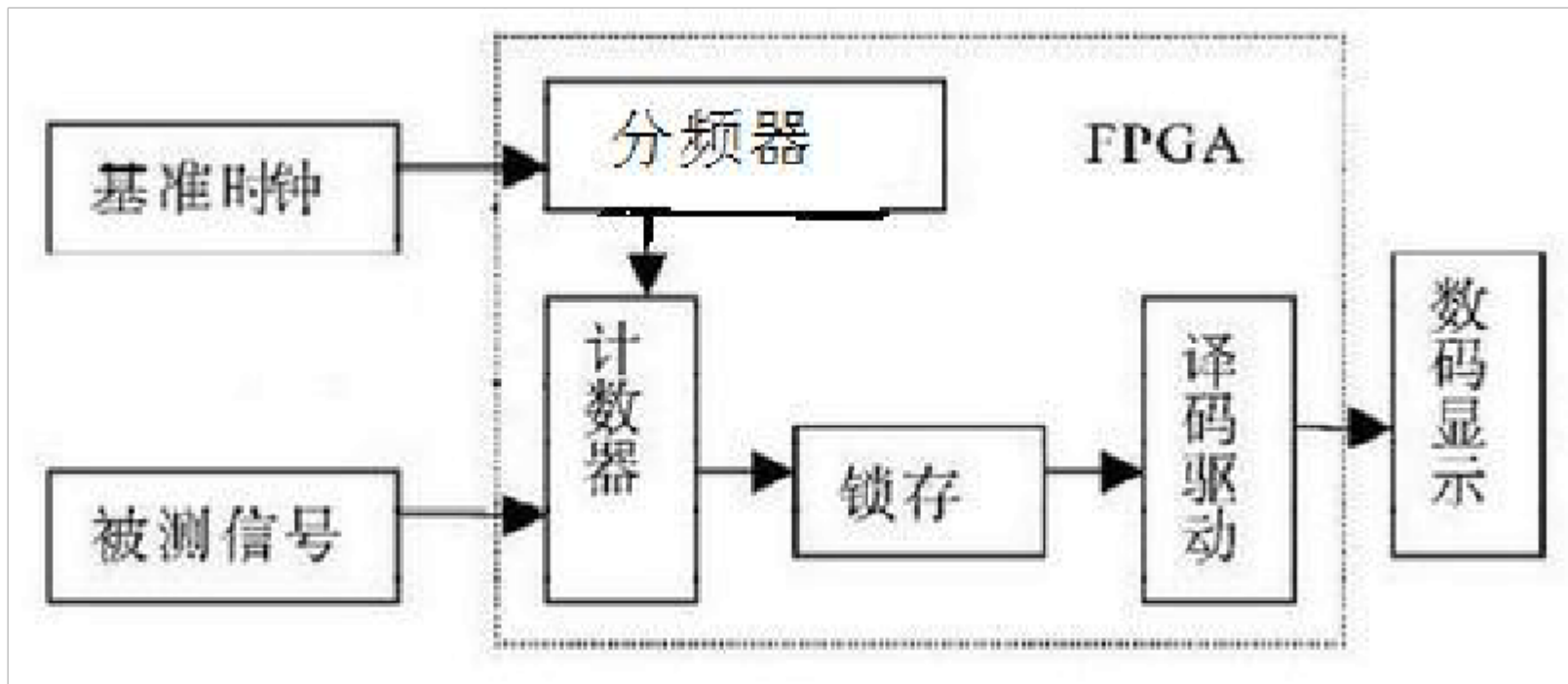

分频器模块

 时钟信号源输出的时钟信号频率高达**50MHz**,经过分频器将其分频为**1Hz**、**4Hz**、**500Hz**和**1000Hz**时钟信号。这四种信号再经过1/2分频,得到时间基准信号,其中**1000Hz**的时钟基准信号用于动态扫描译码电路,**1Hz**的时钟基准信号用于计数器的始能信号。




```

library ieee;
use ieee.std_logic_1164.all;
entity fenpin is
    port( clk: in  std_logic;--50MHz
          clk1: out std_logic;--1Hz
          clk2: out std_logic;--4Hz
          clk3: out std_logic;--500hz
          clk4: out std_logic --1khz
        );
end fenpin;
architecture arch of fenpin is
begin
    process(clk)
        variable cnt1: integer range 0 to 499999999;
        variable cnt2: integer range 0 to 124999999;
        variable cnt3: integer range 0 to 99999;
        variable cnt4: integer range 0 to 49999;
        variable x1,x2,x3,x4: std_logic:='0';
    begin
        if clk'event and clk='1' then
            if cnt1<499999999 then

```

```

                cnt1:=cnt1+1;
            else
                cnt1:=0;  x1:=not x1;
            end if;
            if cnt2<124999999 then
                cnt2:=cnt2+1;
            else
                cnt2:=0;  x2:=not x2;
            end if;
            if cnt3<99999 then
                cnt3:=cnt3+1;
            else
                cnt3:=0; x3:=not x3;
            end if;
            if cnt4<49999 then
                cnt4:=cnt4+1;
            else
                cnt4:=0; x4:=not x4;
            end if;
        end if;
        clk1<=x1;
        clk2<=x2;
        clk3<=x3;
        clk4<=x4;
    end process;
end arch;

```

计数器模块

计数器模块始能端`door`输入分频器模块分频出的0.5Hz 为基准时钟信号频率。计数器`sig`输入待测信号与基准时钟信号进行比较，并且计数。`q0[3..0]`对应的是个位输出，`q1[3..0]`对应的是十位输出，`q2[3..0]`对应的是百位输出，`q3[3..0]`对应的是千位输出。

